

ELECTRICAL POWER TRANSMISSION AND DISTRIBUTION

EE / EEE , 5TH
MOD- IV

Mamaj Ku. Pradhan
SCE, EE, RU.

MCQ

- ① A transmission line has self and mutual impedance of 0.8 PU and 0.2 PU. Find positive negative and zero sequence impedance.
- (A) 0.6, 0.8 and 1.2 PU. Hint: $Z_0 = \frac{Z}{3} + 2Z_m$
- (B) 0.6, 0.6 and 1.2 PU. $Z_1 = \frac{Z}{2} = \frac{Z - Z_m}{3}$
- (C) 0.8, 0.8 and 1.2 PU
- (D) 0.8, 0.6 and 0.4 PU.
2. Positive, negative and zero sequence impedance of line are 2.2 and 5 PU respectively. Find self and mutual impedance respectively.
- (A) 1 and 3 PU (B) 3 and 1 PU
- (C) 2 and 2 PU (D) 2 and 5 PU.
3. For symmetrical network, the neutral current is
 (A) zero (B) & (C) maximum (D) any of these.
4. When a reactance ~~to~~ grounding is used in network, the voltage between Neutral and ground is
 (A) $I_N \cdot X_N$ (B) $I_{R0} \cdot X_n$ (C) $3I_{R0} \cdot X_n$ (D) both B & C.


5. The value of inductance used for compensation of arcing ground is

- (A) $3\omega^2 c$ (B) $\frac{1}{3}\omega^2 c$ (C) $\frac{3}{\omega^2 c}$ (D) $\omega^2 c/3$

6. Earth Fault relay uses the which of Following Sequence current

- (A) Positive sequence (B) Negative sequence
(C) Zero sequence (D) any of above.

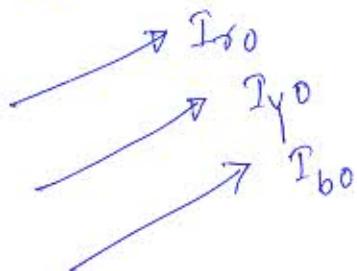7. Which sequence component is represented by the following phasor.



- (A) Positive sequence (B) Zero sequence.
(C) Negative sequence (D) None of these.

8. what is the value of $(1+\alpha+\alpha^2)$?

- (A) 0 (B) 1 (C) -1 (D) ∞

7. in Above Question (a-b) what is Zero Sequence Current.

$$\begin{aligned}
 \text{Ans: } \vec{I}_0 &= \frac{1}{3} [\vec{I}_R + \vec{I}_Y + \vec{I}_B] \\
 &= \frac{1}{3} [100 \angle 30^\circ + 50 \angle 30^\circ + 30 \angle 110^\circ] \\
 &= \frac{1}{3} [81.6 + j6.7] = 27.2 + j2.23 \\
 &\quad \qquad \qquad \qquad \underline{\qquad\qquad\qquad} \\
 &= 27.29 \angle 4.68^\circ A
 \end{aligned}$$

8. Prove that $\frac{1-a^2}{a-a^2} = -a$

$$\begin{aligned}
 \text{Ans: } \frac{1-a^2}{a-a^2} &= \frac{(1+a)(1-a)}{a(1-a)} = \frac{1+a}{a} (1+a+a^2=0) \\
 &= -\frac{a^2}{a} = -a
 \end{aligned}$$

- ⑨ What is the value of zero sequence current
- a. 3 times the current in the neutral wire.
 - b. $\frac{1}{3}$ times of the current in neutral wire.
 - c. $\sqrt{3}$ times the current in the neutral wire.
 - d. Equal to current in the neutral wire

⑩ The tre sequence current is always equal to _____

- a. Always zero
- b. $\frac{1}{3}$ of the negative seq. current
- c. negative sequence current
- d. 3 times of -ve

Short Question and Answer

Q-1 What is unsymmetrical fault?

Ans: Those fault on the power system which gives rise to unsymmetrical fault current i.e. unequal fault current in line with unequal phase displacement.

Q-2 What is the sequence impedance of Transformer?

Ans: Positive Sequence Impedance = Negative Sequence Impedance.

Zero Sequence Impedance = Positive Sequence Impedance
if there is circuit for earth current.

= ∞ , if there is no through cut for earth current.

3. What is the significance of operator \hat{a} ?

Ans: The operator \hat{a} is one which when multiplied to a vector rotates the vector through 120° in anticlock-wise direction.

$$\boxed{\hat{a}I = I[120^\circ]}$$

4. What are the examples of unsymmetrical fault?

Ans:- The different types of unsymmetrical faults are

- L-G fault.
- L-L fault.
- L-L-G fault.

5. What will be the value of zero sequence current in 3ϕ , 4 wire unbalanced system.

Ans:- Zero sequence current = $\frac{1}{3}$ [current in Neutral wire]

6. In a 3 phase 4-wire system, the current in R, Y and B line under abnormal condition of loading are as under.

$$I_R^{\rightarrow} = 100 \angle 30^\circ A, I_Y^{\rightarrow} = 50 \angle 300^\circ A, I_B^{\rightarrow} = 30 \angle 180^\circ A.$$

a) calculate the seq. current.

$$\begin{aligned} I^{\rightarrow} &= \frac{1}{3} [I_R^{\rightarrow} + \alpha I_Y^{\rightarrow} + \alpha^2 I_B^{\rightarrow}] \\ &= \frac{1}{3} [100 \angle 30^\circ + 1.120 \times 50 \angle 300^\circ + 1.120 \times 30 \angle 180^\circ] \\ &= \frac{1}{3} [126.6 + j119.28] \\ &= (42.2 + j39.76) = 57.98 \angle 43.3^\circ A. \end{aligned}$$

Long Question and Answer

- ① Derive the expression of fault in line-ground fault.


Explanation:-

Consider a 3-phase system with an earthed neutral. Let a single line-to-ground fault occurs on the red phase.

under fault condition

$$V_R = 0, I_B = I_f = 0$$

$$I_R = I_0 + I_1 + I_2 = 3I_f$$

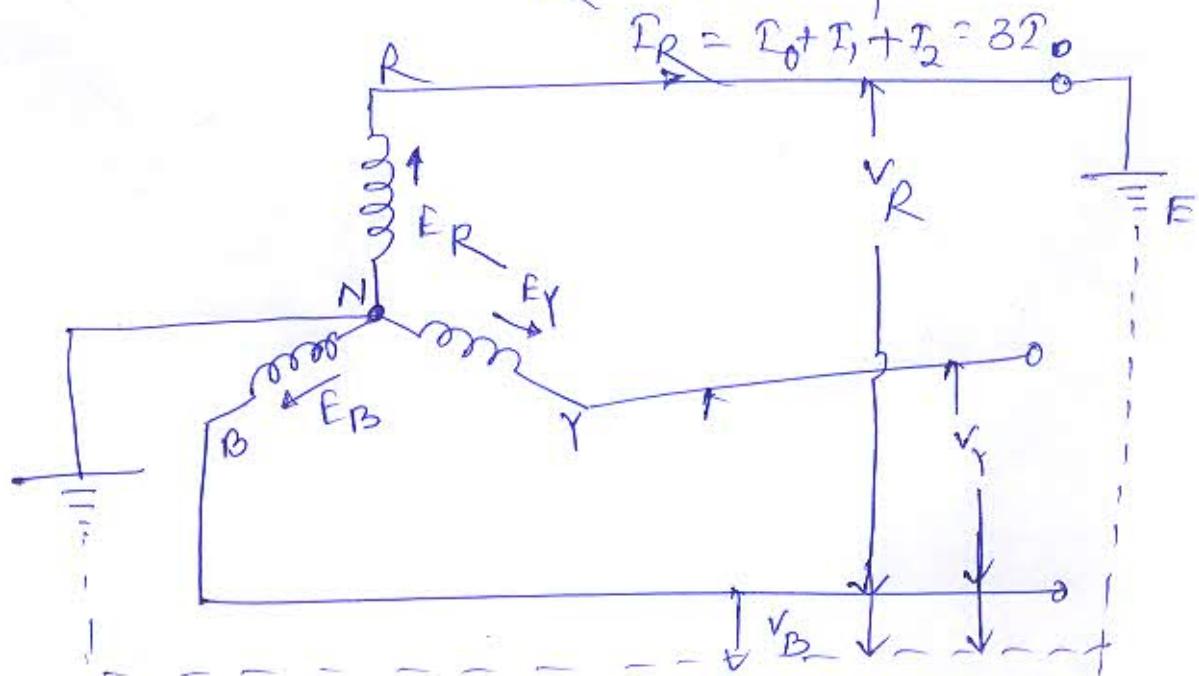

The Sequence Current in red phase in terms of line current

$$\vec{I}_0 = \frac{1}{3} (\vec{I}_R + \vec{I}_Y + \vec{I}_B) = \frac{1}{3} \vec{I}_R$$

$$\vec{I}_1 = \frac{1}{3} (\vec{I}_R + \alpha \vec{I}_Y + \alpha^2 \vec{I}_B) = \frac{1}{3} \vec{I}_R$$

$$\vec{I}_2 = \frac{1}{3} (\vec{I}_R + \alpha^2 \vec{I}_Y + \alpha \vec{I}_B) = \frac{1}{3} \vec{I}_R$$

$$\vec{I}_0 = \vec{I}_1 - \vec{I}_2 = \frac{1}{3} \vec{I}_R$$

Fault Current:-

Let \vec{z}_1, \vec{z}_2 and \vec{z}_0 be the +ve, -ve and zero sequence network. Consider closed loop NRN applying KVL to above circuit.

$$\vec{E}_R = \vec{I}_1 \vec{z}_1 + \vec{I}_2 \vec{z}_2 + \vec{I}_0 \vec{z}_0 + \vec{v}_R$$

as $\vec{v}_R = 0$ and $\vec{I}_1 = \vec{I}_2 = \vec{I}_0$

$$\therefore \vec{E}_R = \vec{I}_0 (\vec{z}_1 + \vec{z}_2 + \vec{z}_0)$$

$$\vec{I}_0 = \frac{\vec{E}_R}{\vec{z}_1 + \vec{z}_2 + \vec{z}_0}$$


$$\text{Fault current } \vec{I}_R = 3 \vec{I}_0 = 3 \cdot \frac{\vec{E}_R}{\vec{z}_1 + \vec{z}_2 + \vec{z}_0}$$

Q2. Write short notes on neutral grounding.

Explanation:-

The process of connecting neutral point of 3-phase system to earth either directly or through some circuit element (Resistance, Reactance) is called neutral grounding.

Fig

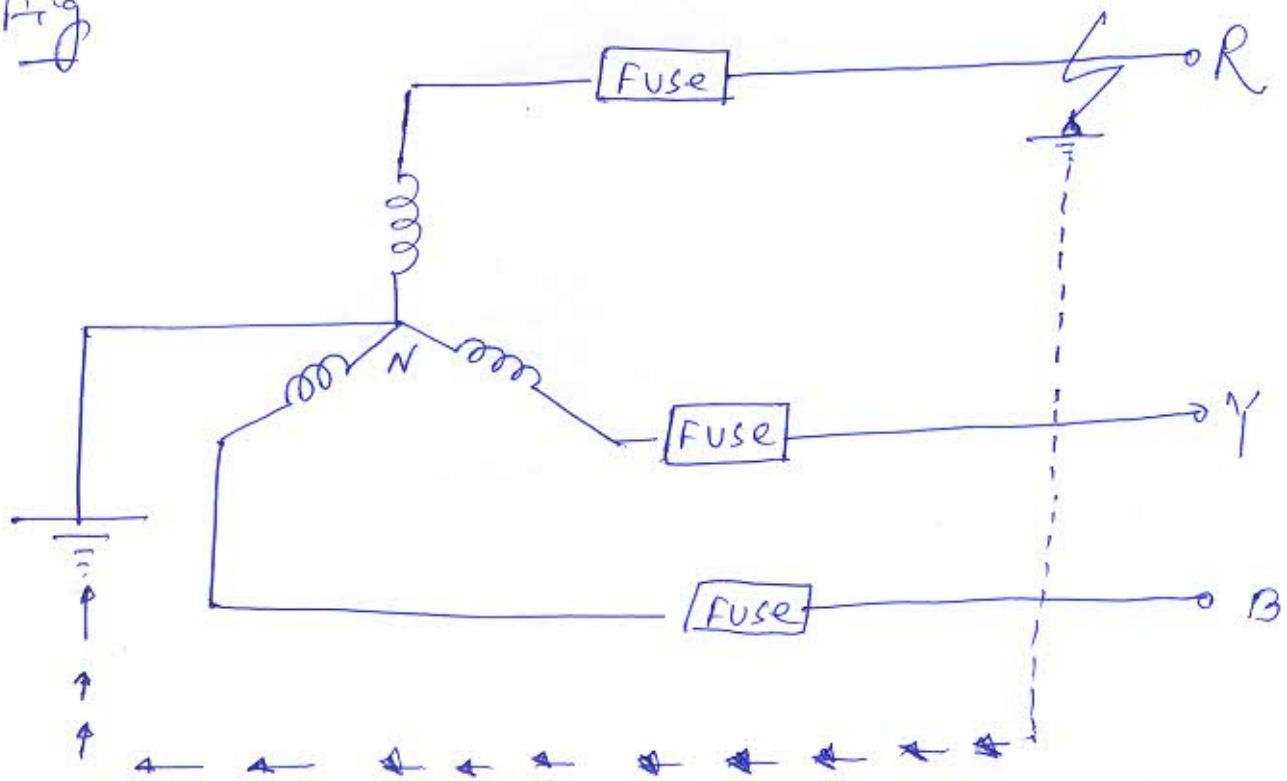

The figure shows, Star connected system with neutral earthed. Suppose a single line to ground fault occurs in line R at point F. This will cause the current to flow through a ground path. Note that current flows from R-phase to earth then to neutral point N and back to R-phase.

Since the impedance of the current path is low, a large current flow through this path. This large current will blow the fuse in R-Phase and isolate the faulty line R.

Advantage:-

- ① The high voltage due to arcing ground are eliminated.
- ② It provide improved service reliability.
- ③ The over voltage due to lightning are discharged to earth.