

# SRINIX COLLEGE OF ENGINEERING, BALASORE

## PROBABLE QUESTIONS AND ANSWERS

### SUBJECT-BETC (2nd semester)

**Q1. A semiconductor is formed by ..... bonds.**

1. Covalent
2. Electrovalent
3. Co-ordinate
4. None of the above

**Answer : 1**

**2. A semiconductor has ..... temperature coefficient of resistance.**

1. Positive
2. Zero
3. Negative
4. None of the above

**Answer : 3**

**Q3. The most commonly used semiconductor is .....**

1. Germanium
2. Silicon
3. Carbon
4. Sulphur

**Answer : 2**

**Q4. A semiconductor has generally ..... valence electrons.**

1. 2
2. 3
3. 6
4. 4

**Answer : 4**

**Q5. The resistivity of pure germanium under standard conditions is about .....**

1.  $6 \times 10^4$
2.  $\Omega \text{ cm}$
3. 60
4.  $\Omega \text{ cm}$
5.  $3 \times 10^6$
6.  $\Omega \text{ cm}$
7.  $6 \times 10^{-4}$
8.  $\Omega \text{ cm}$

**Answer : 2**

**Q6. The resistivity of a pure silicon is about .....**

1.  $100 \Omega \text{ cm}$
2.  $6000 \Omega \text{ cm}$
3.  $3 \times 10^5 \Omega \text{ m}$
4.  $6 \times 10^{-8} \Omega \text{ cm}$

**Answer : 2**

**Q7. When a pure semiconductor is heated, its resistance .....**

1. Goes up
2. Goes down
3. Remains the same
4. Can't say

**Answer : 2**

**Q8. The strength of a semiconductor crystal comes from .....**

1. Forces between nuclei
2. Forces between protons
3. Electron-pair bonds
4. None of the above

**Answer : 3**

**Q9. When a pentavalent impurity is added to a pure semiconductor, it becomes .....**

1. An insulator
2. An intrinsic semiconductor
3. p-type semiconductor
4. n-type semiconductor

**Answer : 4**

**Q10. Addition of pentavalent impurity to a semiconductor creates many .....**

1. Free electrons
2. Holes
3. Valence electrons
4. Bound electrons

**Answer : 1**

**Q11. A pentavalent impurity has ..... Valence electrons**

1. 3
2. 5
3. 4
4. 6

**Answer : 2**

**A12. An n-type semiconductor is .....**

1. Positively charged
2. Negatively charged
3. Electrically neutral
4. None of the above

**Answer : 3**

**Q13. A trivalent impurity has ..... valence electrons**

1. 4
2. 5
3. 6
4. 3

**Answer : 4**

**A14. Addition of trivalent impurity to a semiconductor creates many .....**

1. Holes
2. Free electrons
3. Valence electrons
4. Bound electrons

**Answer : 1**

**Q15. A hole in a semiconductor is defined as .....**

1. A free electron
2. The incomplete part of an electron pair bond

3. A free proton
4. A free neutron

**Answer : 2**

**Q16. The impurity level in an extrinsic semiconductor is about ..... of pure semiconductor.**

1. 10 atoms for  $10^8$  atoms
2. 1 atom for  $10^8$  atoms
3. 1 atom for  $10^4$  atoms
4. 1 atom for 100 atoms

**Answer : 2**

**Q17. As the doping to a pure semiconductor increases, the bulk resistance of the semiconductor .....**

1. Remains the same
2. Increases
3. Decreases
4. None of the above

**Answer : 3**

**Q18. A hole and electron in close proximity would tend to .....**

1. Repel each other
2. Attract each other
3. Have no effect on each other
4. None of the above

**Answer : 2**

**Q19. In a semiconductor, current conduction is due to .....**

1. Only holes
2. Only free electrons
3. Holes and free electrons
4. None of the above

**Answer : 3**

**Q20. The random motion of holes and free electrons due to thermal agitation is called .....**

1. Diffusion
2. Pressure
3. Ionisation
4. None of the above

**Answer : 1**

**21. A forward biased pn junction diode has a resistance of the order of**

1.  $\Omega$
2.  $k\Omega$
3.  $M\Omega$
4. None of the above

**Answer : 1**

**Q22. The battery connections required to forward bias a pn junction are .....**

1. +ve terminal to p and -ve terminal to n
2. -ve terminal to p and +ve terminal to n
3. -ve terminal to p and -ve terminal to n
4. None of the above

**Answer : 1**

**Q23. The barrier voltage at a pn junction for germanium is about .....**

3. 5 V
4. 3 V
5. Zero

6. 3 V

**Answer : 4**

**Q24. In the depletion region of a pn junction, there is a shortage of .....**

1. Acceptor ions
2. Holes and electrons
3. Donor ions
4. None of the above

**Answer : 2**

**Q25. A reverse bias pn junction has .....**

1. Very narrow depletion layer
2. Almost no current
3. Very low resistance
4. Large current flow

**Answer : 2**

**Q26. A pn junction acts as a .....**

1. Controlled switch
2. Bidirectional switch
3. Unidirectional switch
4. None of the above

**Answer : 3**

**Q27. A reverse biased pn junction has resistance of the order of**

1.  $\Omega$
2.  $k\Omega$
3.  $M\Omega$
4. None of the above

**Answer : 3**

**Q28. The leakage current across a pn junction is due to .....**

1. Minority carriers
2. Majority carriers
3. Junction capacitance
4. None of the above

**Answer : 1**

**Q29. When the temperature of an extrinsic semiconductor is increased, the pronounced effect is on.....**

1. Junction capacitance
2. Minority carriers
3. Majority carriers
4. None of the above

**Answer : 2**

**Q30. With forward bias to a pn junction , the width of depletion layer .....**

1. Decreases
2. Increases
3. Remains the same
4. None of the above

**Answer : 1**

**Q31. The leakage current in a pn junction is of the order of**

1. Aa
2. mA
3. kA
4.  $\mu A$

**Answer : 4**

**Q32. In an intrinsic semiconductor, the number of free electrons .....**

1. Equals the number of holes
2. Is greater than the number of holes
3. Is less than the number of holes
4. None of the above

**Answer : 1**

**Q33. At room temperature, an intrinsic semiconductor has .....**

1. Many holes only
2. A few free electrons and holes
3. Many free electrons only
4. No holes or free electrons

**Answer : 2**

**Q34. At absolute temperature, an intrinsic semiconductor has .....**

1. A few free electrons
2. Many holes
3. Many free electrons
4. No holes or free electrons

**Answer : 4**

**Q35. At room temperature, an intrinsic silicon crystal acts approximately as .....**

1. A battery
2. A conductor
3. An insulator
4. A piece of copper wire

**Answer : 3**

**Q36. Under normal conditions a diode conducts current when it is .....**

1. reverse biased
2. forward biased
3. avalanched
4. saturated

**Answer : 2**

**Q37. The term bias in electronics usually means .....**

1. the value of ac voltage in the signal.
2. the condition of current through a pn junction.
3. the value of dc voltages for the device to operate properly.
4. the status of the diode.

**Answer : 3**

**38. A crystal diode has .....**

1. one pn junction
2. two pn junctions
3. three pn junctions
4. none of the above

**Answer : 1**

**39. A crystal diode has forward resistance of the order of .....**

1.  $k\Omega$
2.  $\Omega$
3.  $M\Omega$
4. none of the above

**Answer : 2**

**Q40. If the arrow of crystal diode symbol is positive w.r.t. bar, then diode is ..... biased.**

1. forward
2. reverse
3. either forward or reverse

4. none of the above

**Answer : 1**

**Q41. The reverse current in a diode is of the order of .....**

1. kA
2. mA
3.  $\mu$ A
4. A

**Answer : 3**

**Q42. The forward voltage drop across a silicon diode is about .....**

1. 2.5 V
2. 3 V
3. 10 V
4. 0.7 V

**Answer : 4**

**Q43. A crystal diode is used as .....**

1. an amplifier
2. a rectifier
3. an oscillator
4. a voltage regulator

**Answer : 2**

**Q44. The d.c. resistance of a crystal diode is ..... its a.c. resistance**

1. the same as
2. more than
3. less than
4. none of the above

**Answer : 3**

**Q45. An ideal crystal diode is one which behaves as a perfect ..... when forward biased.**

1. conductor
2. insulator
3. resistance material
4. none of the above

**Answer : 1**

**Q46. The ratio of reverse resistance and forward resistance of a germanium crystal diode is about .....**

1. 1 : 1
2. 100 : 1
3. 1000 : 1
4. 40,000 : 1

**Answer : 4**

**Q 47. The leakage current in a crystal diode is due to .....**

1. minority carriers
2. majority carriers
3. junction capacitance
4. none of the above

**Answer :1**

**Q48. If the temperature of a crystal diode increases, then leakage current .....**

1. remains the same
2. decreases
3. increases
4. becomes zero

**Answer :3**

**Q49. The PIV rating of a crystal diode is ..... that of equivalent vacuum diode**



1. the same as
2. lower than
3. more than
4. none of the above

**Answer :2**

**Q50. If the doping level of a crystal diode is increased, the breakdown voltage.....**

1. remains the same
2. is increased
3. is decreased
4. none of the above

**Answer :3**

**Q51. The knee voltage of a crystal diode is approximately equal to .....**

1. applied voltage
2. breakdown voltage
3. forward voltage
4. barrier potential

**Answer :4**

**Q52. When the graph between current through and voltage across a device is a straight line, the device is referred to as .....**

1. linear
2. active
3. nonlinear
4. passive

**Answer :1**

**Q53. When the crystal current diode current is large, the bias is .....**

1. forward
2. inverse
3. poor
4. reverse

**Answer :1**

**Q54. A crystal diode is a ..... device**

1. non-linear
2. bilateral
3. linear
4. none of the above

**Answer :1**

**Q55. A crystal diode utilises ..... characteristic for rectification**

1. reverse
2. forward
3. forward or reverse
4. none of the above

**Answer :2**

**Q56. When a crystal diode is used as a rectifier, the most important consideration is .....**

1. forward characteristic
2. doping level
3. reverse characteristic
4. PIC rating

**Answer :4**

**Q57. If the doping level in a crystal diode is increased, the width of depletion layer.....**

1. remains the same
2. is decreased

3. in increased
4. none of the above

**Answer :3**

**Q58. A zener diode has .....**

1. one pn junction
2. two pn junctions
3. three pn junctions
4. none of the above

**Answer :1**

**Q59. A zener diode is used as .....**

1. an amplifier
2. a voltage regulator
3. a rectifier
4. a multivibrator

**Answer :2**

**Q60. The doping level in a zener diode is ..... that of a crystal diode**

1. the same as
2. less than
3. more than
4. none of the above

**Answer :3**

**Q61. A zener diode is always ..... connected.**

1. reverse
2. forward
3. either reverse or forward
4. none of the above

**Answer :1**

**Q62. A zener diode utilizes ..... characteristics for its operation.**

1. forward
2. reverse
3. both forward and reverse
4. none of the above

**Answer :2**

**Q63. In the breakdown region, a zener diode behaves like a ..... source.**

1. constant voltage
2. constant current
3. constant resistance
4. none of the above

**Answer :1**

**Q64. A zener diode is destroyed if it.....**

1. is forward biased
2. is reverse biased
3. carries more than rated current
4. none of the above

**Answer :3**

**Q65. A series resistance is connected in the zener circuit to.....**

1. properly reverse bias the zener
2. protect the zener
3. properly forward bias the zener
4. none of the above

**Answer :2**

**Q66. A zener diode is ..... device**



1. a non-linear
2. a linear
3. an amplifying
4. none of the above

**Answer :1**

**Q67. A zener diode has ..... breakdown voltage**

1. undefined
2. sharp
3. zero
4. none of the above

**Answer :2**

**Q68. .... rectifier has the lowest forward resistance**

1. solid state
2. vacuum tube
3. gas tube
4. none of the above

**Answer :1**

**Q69. Mains a.c. power is converted into d.c. power for .....**

1. lighting purposes
2. heaters
3. using in electronic equipment
4. none of the above

**Answer :3**

**Q70. The disadvantage of a half-wave rectifier is that the.....**

1. components are expensive
2. diodes must have a higher power rating
3. output is difficult to filter
4. none of the above

**Answer :3**

**Q71. If the a.c. input to a half-wave rectifier is an r.m.s value of  $400/\sqrt{2}$  volts, then diode PIV rating is .....**

1.  $400/\sqrt{2}$  V
2. 400 V
3.  $400 \times \sqrt{2}$  V
4. none of the above

**Answer :2**

**Q72. The ripple factor of a half-wave rectifier is .....**

1. 2
2. 1.21
3. 2.5
4. 0.48

**Answer :2**

**Q73. There is a need of transformer for .....**

1. half-wave rectifier
2. centre-tap full-wave rectifier
3. bridge full-wave rectifier
4. none of the above

**Answer :2**

**Q74. The PIV rating of each diode in a bridge rectifier is ..... that of the equivalent centre-tap rectifier**

1. one-half
2. the same as

3. twice
4. four times

**Answer :1**

**Q75. For the same secondary voltage, the output voltage from a centre-tap rectifier is ..... than that of bridge rectifier**

1. twice
2. thrice
3. four time
4. one-half

**Answer :4**

**Q76. If the PIV rating of a diode is exceeded, .....**

1. the diode conducts poorly
2. the diode is destroyed
3. the diode behaves like a zener diode
4. none of the above

**Answer :2**

**Q77. A 10 V power supply would use ..... as filter capacitor.**

1. paper capacitor
2. mica capacitor
3. electrolytic capacitor
4. air capacitor

**Answer :3**

**Q78. A 1,000 V power supply would use ..... as a filter capacitor**

1. paper capacitor
2. air capacitor
3. mica capacitor
4. electrolytic capacitor

**Answer :1**

**Q79. The ..... filter circuit results in the best voltage regulation**

1. choke input
2. capacitor input
3. resistance input
4. none of the above

**Answer :1**

**Q80. A half-wave rectifier has an input voltage of 240 V r.m.s. If the step-down transformer has a turns ratio of 8:1, what is the peak load voltage? Ignore diode drop.**

1. 27.5 V
2. 86.5 V
3. 30 V
4. 42.5 V

**Answer :4**

**Q81. The maximum efficiency of a half-wave rectifier is .....**

1. 40.6 %
2. 81.2 %
3. 50 %
4. 25 %

**Answer :1**

**Q82. The most widely used rectifier is .....**

1. half-wave rectifier
2. centre-tap full-wave rectifier
3. bridge full-wave rectifier
4. none of the above

**Answer :3**

**Q83. A transistor has .....**

1. one pn junction
2. two pn junctions
3. three pn junctions
4. four pn junctions

**Answer : 2**

**Q84.The number of depletion layers in a transistor is .....**

1. four
2. three
3. one
4. two

**Answer : 4**

**Q85.. The base of a transistor is ..... doped**

1. heavily
2. moderately
3. lightly
4. none of the above

**Answer : 3**

**Q86. The element that has the biggest size in a transistor is .....**

1. collector
2. base
3. emitter
4. collector-base-junction

**Answer : 1**

**Q87. In a pnp transistor, the current carriers are .....**

1. acceptor ions
2. donor ions
3. free electrons
4. holes

**Answer : 4**

**Q88. The collector of a transistor is ..... doped**

1. heavily
2. moderately
3. lightly
4. none of the above

**Answer : 2**

**Q88. A transistor is a ..... operated device**

1. current
2. voltage
3. both voltage and current
4. none of the above

**Answer : 1**

**Q89. In a npn transistor, ..... are the minority carriers**

1. free electrons
2. holes
3. donor ions
4. acceptor ions

**Answer : 2**

**Q90. The emitter of a transistor is ..... doped**

1. lightly
2. heavily

3. moderately
4. none of the above

**Answer : 2**

**Q91. In a transistor, the base current is about ..... of emitter current**

1. 25%
2. 20%
3. 35 %
4. 5%

**Answer : 4**

**Q92. At the base-emitter junctions of a transistor, one finds .....**

1. a reverse bias
2. a wide depletion layer
3. low resistance
4. none of the above

**Answer : 3**

**Q93. The input impedance of a transistor is .....**

1. high
2. low
3. very high
4. almost zero

**Answer : 2**

**Q94. Most of the majority carriers from the emitter .....**

1. recombine in the base
2. recombine in the emitter
3. pass through the base region to the collector
4. none of the above

**Answer :3**

**Q95. The current  $I_B$  is .....**

1. electron current
2. hole current
3. donor ion current
4. acceptor ion current

**Answer : 1**

**Q96. In a transistor .....**

$$I_C = I_E + I_B$$

$$I_B = I_C + I_E$$

$$I_E = I_C - I_B$$

$$I_E = I_C + I_B$$

**Answer : 4**

**Q97. The value of  $\alpha$  of a transistor is .....**

- more than 1
- less than 1
- 1
- none of the above

**Answer : 2**

**Q98.  $I_C = \alpha I_E + \dots\dots\dots$**

1.  $I_B$
2.  $I_{CEO}$
3.  $I_{CBO}$
4.  $\beta I_B$

**Answer : 3**

**Q99. The output impedance of a transistor is .....**

1. high
2. zero
3. low
4. very low

**Answer : 1**

**Q100. In a transistor,  $I_C = 100$  mA and  $I_E = 100.2$  mA. The value of  $\beta$  is .....**

1. 100
2. 50
3. about 1
4. 200

**Answer : 4**

**Q101. In a transistor if  $\beta = 100$  and collector current is 10 mA, then  $I_E$  is .....**

1. 100 mA
2. 100.1 mA
3. 110 mA
4. none of the above

**Answer : 2**

**Q102. The relation between  $\beta$  and  $\alpha$  is .....**

1.  $\beta = 1 / (1 - \alpha)$
2.  $\beta = (1 - \alpha) / \alpha$
3.  $\beta = \alpha / (1 - \alpha)$
4.  $\beta = \alpha / (1 + \alpha)$

**Answer : 3**

**Q103. The value of  $\beta$  for a transistor is generally .....**

1. 1
2. less than 1
3. between 20 and 500
4. above 500

**Answer : 3**

**Q103. The most commonly used transistor arrangement is ..... arrangement**

1. common emitter
2. common base
3. common collector
4. none of the above

**Answer : 1**

**Q104. The input impedance of a transistor connected in ..... arrangement is the highest**

1. common emitter
2. common collector
3. common base
4. none of the above

**Answer : 2**

**Q105. The output impedance of a transistor connected in ..... arrangement is the highest**

1. common emitter
2. common collector
3. common base
4. none of the above

**Answer : 3**

**Q106. The phase difference between the input and output voltages in a common base arrangement is .....**

1.  $180^\circ$

2.  $90^\circ$
3.  $270^\circ$
4.  $0^\circ$

**Answer : 4**

**Q107. The power gain in a transistor connected in ..... arrangement is the highest**

1. common emitter
2. common base
3. common collector
4. none of the above

**Answer : 1**

**Q108. The phase difference between the input and output voltages of a transistor connected in common emitter arrangement is .....**

1.  $0^\circ$
2.  $180^\circ$
3.  $90^\circ$
4.  $270^\circ$

**Answer : 2**

**Q109. The voltage gain in a transistor connected in ..... arrangement is the highest**

1. common base
2. common collector
3. common emitter
4. none of the above

**Answer : 3**

**Q110. As the temperature of a transistor goes up, the base-emitter resistance .....**

1. decreases
2. increases
3. remains the same
4. none of the above

**Answer : 1**

**Q111. The voltage gain of a transistor connected in common collector arrangement is .....**

1. equal to 1
2. more than 10
3. more than 100
4. less than 1

**Answer : 4**

**Q112. The phase difference between the input and output voltages of a transistor connected in common collector arrangement is .....**

1.  $180^\circ$
2.  $0^\circ$
3.  $90^\circ$
4.  $270^\circ$

**Answer : 2**

**Q113.  $I_C = \beta I_B + \dots\dots\dots$**

1.  $I_{CBO}$
2.  $I_C$
3.  $I_{CEO}$
4.  $\alpha I_E$

**Answer : 3**

**Q114.  $I_C = [\alpha / (1 - \alpha)] I_B + \dots\dots\dots$**

1.  $I_{CEO}$



2.  $I_{CBO}$
3.  $I_C$
4.  $(1 - \alpha) I_B$

**Answer : 1**

**Q115.**  $I_C = [\alpha / (1 - \alpha)] I_B + [..... / (1 - \alpha)]$

1.  $I_{CBO}$
2.  $I_{CEO}$
3.  $I_C$
4.  $I_E$

**Answer : 1**

**Q116.** BC 147 transistor indicates that it is made of .....

1. germanium
2. silicon
3. carbon
4. none of the above

**Answer : 2**

**Q117.**  $I_{CEO} = (.....) I_{CBO}$

1.  $\beta$
2.  $1 + \alpha$
3.  $1 + \beta$
4. none of the above

**Answer : 3**

**Q118.** A transistor is connected in CB mode. If it is not connected in CE mode with same bias voltages, the values of  $I_E$ ,  $I_B$  and  $I_C$  will .....

1. remain the same
2. increase
3. decrease
4. none of the above

**Answer : 1**

**Q119.** If the value of  $\alpha$  is 0.9, then value of  $\beta$  is .....

1. 9
2. 0.9
3. 900
4. 90

**Answer : 4**

**Q120.** In a transistor, signal is transferred from a ..... circuit

1. high resistance to low resistance
2. low resistance to high resistance
3. high resistance to high resistance
4. low resistance to low resistance

**Answer : 2**

**Q121.** The arrow in the symbol of a transistor indicates the direction of .....

1. electron current in the emitter
2. electron current in the collector
3. hole current in the emitter
4. donor ion current

**Answer : 3**

**Q122.** The leakage current in CE arrangement is ..... that in CB arrangement

1. more than
2. less than
3. the same as
4. none of the above

**Answer : 1**

**Q.123. Transistor biasing represents ..... conditions**

1. a.c.
2. d.c.
3. both a.c. and d.c.
4. none of the above

**Answer : 2**

**Q.124. Transistor biasing is done to keep ..... in the circuit**

1. Proper direct current
2. Proper alternating current
3. The base current small
4. Collector current small

**Answer : 1**

**Q125. Operating point represents .....**

1. Values of  $I_C$  and  $V_{CE}$  when signal is applied
2. The magnitude of signal
3. Zero signal values of  $I_C$  and  $V_{CE}$
4. None of the above

**Answer : 3**

**Q126. If biasing is not done in an amplifier circuit, it results in .....**

1. Decrease in the base current
2. Unfaithful amplification
3. Excessive collector bias
4. None of the above

**Answer : 2**

**Q127. Transistor biasing is generally provided by a .....**

1. Biasing circuit
2. Bias battery
3. Diode
4. None of the above

**Answer : 1**

**Q128. For faithful amplification by a transistor circuit, the value of  $V_{BE}$  should ..... for a silicon transistor**

1. Be zero
2. Be 0.01 V
3. Not fall below 0.7 V
4. Be between 0 V and 0.1 V

**Answer : 3**

**Q129. For proper operation of the transistor, its collector should have .....**

1. Proper forward bias
2. Proper reverse bias
3. Very small size
4. None of the above

**Answer : 2**

**Q130. For faithful amplification by a transistor circuit, the value of  $V_{CE}$  should ..... for silicon transistor**

1. Not fall below 1 V
2. Be zero
3. Be 0.2 V
4. None of the above

**Answer : 1**

**Q131. The circuit that provides the best stabilization of operating point is .....**

1. Base resistor bias
2. Collector feedback bias
3. Potential divider bias
4. None of the above

**Answer : 3**

**Q132. The point of intersection of d.c. and a.c. load lines represents .....**

1. Operating point
2. Current gain
3. Voltage gain
4. None of the above

**Answer : 1**

**Q133. An ideal value of stability factor is .....**

1. 100
2. 200
3. More than 200
4. 1

**Answer : 4**

**Q134. The zero signal  $I_C$  is generally ..... mA in the initial stages of a transistor amplifier**

1. 4
2. 1
3. 3
4. More than 10

**Answer : 2**

**Q135. If the maximum collector current due to signal alone is 3 mA, then zero signal collector current should be at least equal to .....**

1. 6 mA
2. mA
3. 3 mA
4. 1 mA

**Answer : 3**

**Q136. The disadvantage of base resistor method of transistor biasing is that it .....**

1. Is complicated
2. Is sensitive to changes in  $\beta$
3. Provides high stability
4. None of the above

**Answer : 2**

**Q137. The biasing circuit has a stability factor of 50. If due to temperature change,  $I_{CBO}$  changes by 1  $\mu A$ , then  $I_C$  will change by .....**

1. 100  $\mu A$
2. 25  $\mu A$
3. 20  $\mu A$
4. 50  $\mu A$

**Answer : 4**

**Q138. For good stabilisation in voltage divider bias, the current  $I_1$  flowing through  $R_1$  and  $R_2$  should be equal to or greater than**

1. 10  $I_B$
2. 3  $I_B$
3. 2  $I_B$
4. 4  $I_B$

**Answer : 1**

**Q139. The leakage current in a silicon transistor is about ..... the leakage current in a germanium transistor**

1. One hundredth
2. One tenth
3. One thousandth
4. One millionth

**Answer : 3**

**Q140. The operating point is also called the .....**

1. Cut off point
2. Quiescent point
3. Saturation point
4. None of the above

**Answer : 2**

**Q141. For proper amplification by a transistor circuit, the operating point should be located at the ..... of the d.c. load line**

1. The end point
2. Middle
3. The maximum current point
4. None of the above

**Answer : 2**

**Q142. The operating point ..... on the a.c. load line**

1. Also line
2. Does not lie
3. May or may not lie
4. Data insufficient

**Answer : 1**

**Q143. The disadvantage of voltage divider bias is that it has .....**

1. High stability factor
2. Low base current
3. Many resistors
4. None of the above

**Answer : 3**

**Q144. Thermal runaway occurs when .....**

1. Collector is reverse biased
2. Transistor is not biased
3. Emitter is forward biased
4. Junction capacitance is high

**Answer : 2**

**Q145. The purpose of resistance in the emitter circuit of a transistor amplifier is to .....**

1. Limit the maximum emitter current
2. Provide base-emitter bias
3. Limit the change in emitter current
4. None of the above

**Answer : 3**

**Q146. In a transistor amplifier circuit  $V_{CE} = V_{CB} + \dots\dots\dots$**

1.  $V_{BE}$
2.  $2V_{BE}$
3.  $5 V_{BE}$
4. None of the above

**Answer : 1**

**Q147. The base resistor method is generally used in .....**

1. Amplifier circuits
2. Switching circuits
3. Rectifier circuits
4. None of the above

**Answer : 2**

**Q148. For germanium transistor amplifier,  $V_{CE}$  should ..... for faithful amplification**

1. Be zero
2. Be 0.2 V
3. Not fall below 0.7 V
4. None of the above

**Answer : 3**

**Q149. In a base resistor method, if the value of  $\beta$  changes by 50, then collector current will change by a factor .....**

1. 25
2. 50
3. 100
4. 200

**Answer : 2**

**Q150. The stability factor of a collector feedback bias circuit is ..... that of base resistor bias.**

1. The same as
2. More than
3. Less than
4. None of the above

**Answer : 3**

**Q151. In the design of a biasing circuit, the value of collector load  $R_C$  is determined by .....**

1.  $V_{CE}$  consideration
2.  $V_{BE}$  consideration
3.  $I_B$  consideration
4. None of the above

**Answer : 1**

**Q152. If the value of collector current  $I_C$  increases, then the value of  $V_{CE}$  .....**

1. Remains the same
2. Decreases
3. Increases
4. None of the above

**Answer : 2**

**Q153. If the temperature increases, the value of  $V_{CE}$  .....**

1. Remains the same
2. Is increased
3. Is decreased
4. None of the above

**Answer : 3**

**Q154. The stabilisation of operating point in potential divider method is provided by .....**

1.  $R_E$  consideration
2.  $R_C$  consideration
3.  $V_{CC}$  consideration
4. None of the above

**Answer: 1**

**Q155. The value of  $V_{BE}$  .....**

1. Depends upon  $I_C$  to moderate extent
2. Is almost independent of  $I_C$
3. Is strongly dependant on  $I_C$
4. None of the above

**Answer : 2**

**Q156. When the temperature changes, the operating point is shifted due to .....**

1. Change in  $I_{CBO}$
2. Change in  $V_{CC}$
3. Change in the values of circuit resistance
4. None of the above

**Answer : 1**

**Q157. The value of stability factor for a base resistor bias is .....**

1.  $R_B (\beta+1)$
2.  $(\beta+1)R_C$
3.  $(\beta+1)$
4.  $1-\beta$

**Answer : 3**

**Q158. In a particular biasing circuit, the value of  $R_E$  is about .....**

1. 10 k $\Omega$
2. 1 M $\Omega$
3. 100 k $\Omega$
4. 800  $\Omega$

**Answer : 4**

**Q159. A silicon transistor is biased with base resistor method. If  $\beta=100$ ,  $V_{BE}=0.7$  V, zero signal collector current  $I_C = 1$  mA and  $V_{CC} = 6$  V, what is the value of the base resistor  $R_B$ ?**

1. 105 k $\Omega$
2. 530 k $\Omega$
3. 315 k $\Omega$
4. None of the above

**Answer : 2**

**Q160. In voltage divider bias,  $V_{CC} = 25$  V;  $R_1 = 10$  k $\Omega$ ;  $R_2 = 2.2$  k $\Omega$ ;  $R_C = 3.6$  k $\Omega$  and  $R_E = 1$  k $\Omega$ . What is the emitter voltage?**

1. 6.7 V
2. 5.3 V
3. 4.9 V
4. 3.8 V

**Answer : 4**

**Q161. In the above question (Q38.) , what is the collector voltage?**

5. 3 V
6. 8 V
7. 6 V
8. 7 V

**Answer : 1**

**Q162. In voltage divider bias, operating point is 3 V, 2 mA. If  $V_{CC} = 9$  V,  $R_C = 2.2$  k $\Omega$ , what is the value of  $R_E$  ?**

1. 2000  $\Omega$
2. 1400  $\Omega$
3. 800  $\Omega$
4. 1600  $\Omega$

**Answer : 3**



